

APPLICATION NOTE 11

# Programmable Universal Filter Implements C-Message Weighting Function

The C-message filter, which simulates the frequency response of the human ear, is a commonly specified test and measurement filter for voice, audio, and telecommunication applications in the U.S. In Europe, a close relative is a psophometric noise-weighting filter. You can construct either type by cascading three 2nd-order bandpass sections with a 2nd-order lowpass section. The C-message filter, for example, is shown in **Figure 1**

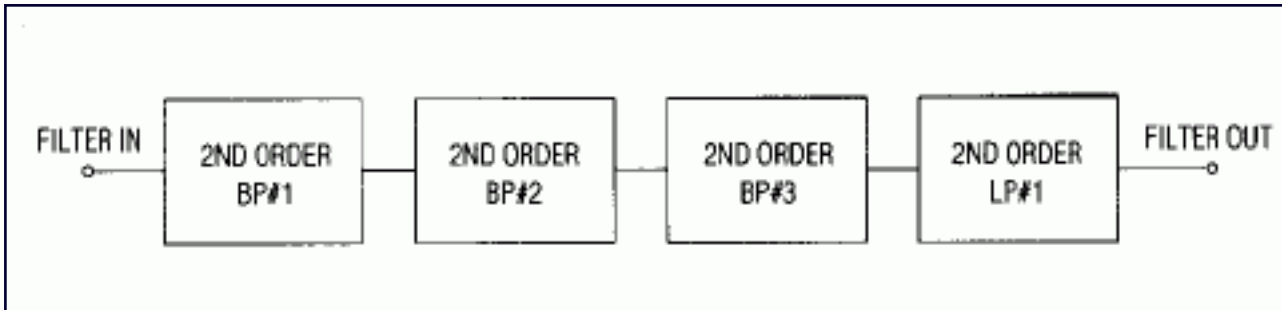



Figure 1. Cascaded, 2nd-order universal filter sections implement a C-message filter.

Dual universal, 2nd-order IC filters provide a compact and efficient means for implementing the circuit of Figure 1. If the IC filters are programmable, switched-capacitor types as shown, you can rapidly implement a C-message, psophometric, or other test filteres on demand simply by loading the chips with different sets of coefficients. These coefficients set each 2nd-order section's filter mode, Q, and cutoff or center frequency  $f_0$ . The C-message filter has poles only, which are specified by the IEEE Standard 743-1984:

Table 1.

Pole	Value in rad/sec	Value in Hz ( $f_0$ )	Q
BP#1	-1502 j1267	312.741	0.6540
BP#2	-2439 j5336	933.761	1.2027
BP#3	-4690 j15267	2541.886	1.7026
LP#1	-4017 j21575	3492.778	2.7316

**Figure 2** shows the external connections that configure two filter ICs in the architecture of Figure 1, along with a table of decimal equivalents for the digital coefficients associated with each filter section. These 2nd-order sections establish pole locations in accordance with the  $f_0$  values listed. Each section contains two continuous-time Chebyshev filters whose center frequency can be digitally programmed in 128 steps over the range 1 to 25kHz. Passband ripple is 0.1dB. For maximum signal-to-noise ratio, the signal amplitude at each section output should be as high as possible.

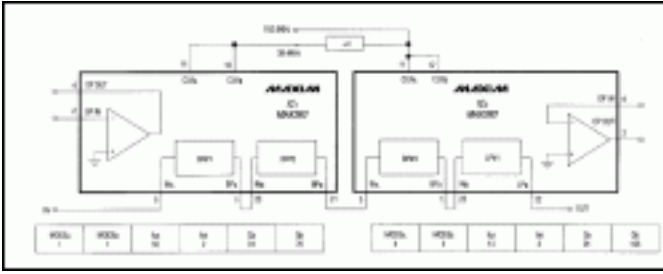


[More Detailed Image](#)

Figure 2. The circuit connections and coefficient sets shown enable two programmable, switched-capacitor filter ICs to realize the C-message filter of Figure 1. By loading the ICs with different coefficient sets, you can obtain the European psophometric noise-weighting filter and other test/measurement filters.

Signal swings are as follows: If you apply 4V to input  $IN_A$  on  $IC_1$ , output  $BP_A$  swings 2.7V, output  $BP_B$  swings 1.85V, output  $BP_A$  of  $IC_2$  swings 1.6V, and the lowpass output ( $LP_A$  of  $IC_2$ ) swings 3.2V.  $IC_2$  operates in mode 4 instead of mode 1, which provides a gain of 2 instead of 1 for the LP and BP outputs (see data sheet)

You must bandlimit the filter's input signal to  $f_{CLK}/4$  or less, where (in this case)  $f_{CLK} = 38.4kHz$ . The uncommitted op amp in  $IC_1$  can provide second- or 3rd-order lowpass filter for this purpose. The uncommitted op amp in  $IC_2$  can provide a similar lowpass filter for smoothing the output signal.

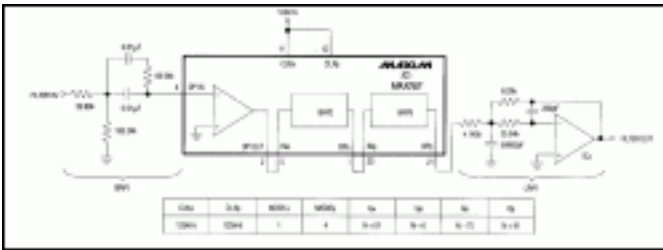As an alternative, you can realize the C-message function using one filter IC and an external op amp (**Figure 3**). This approach lacks flexibility, however. You can no longer switch to other filter functions by electrically reprogramming the circuit.



[More Detailed Image](#)

Figure 3. This circuit, based on one filter IC and an external op amp, produces the same C-message response of Figure 1 but lacks programming flexibility.

This circuit realizes the first bandpass (BP#1) in terms of external resistors and capacitors around uncommitted opamp of  $IC_1$ . BP#1, which also serves as an antialiasing filter for the sampling action of  $IC_1$ , is an infinite-gain, multiple-feedback bandpass filter with  $f_0 = 312.74Hz$ ,  $Q = 0.654$ , and gain = 0.654. Design procedures for this configuration are available in the literature.

$IC_2$  implements BP#2 and BP#3 with the same gain and signal levels as in Figure 1. The external op amp with resistors and capacitors implements LP#1, which also serves as the output smoothing filter. Like BP#1 you can design LP#1 as an infinite-gain, multiple-feedback circuit with  $f_0 = 3492.778Hz$ ,  $Q = 2.7316$ , and gain = 2.

The 125kHz clock frequency is arbitrary; other values require that you program  $IC_1$  for a different  $f_{CLK}/f_0$  ratio.

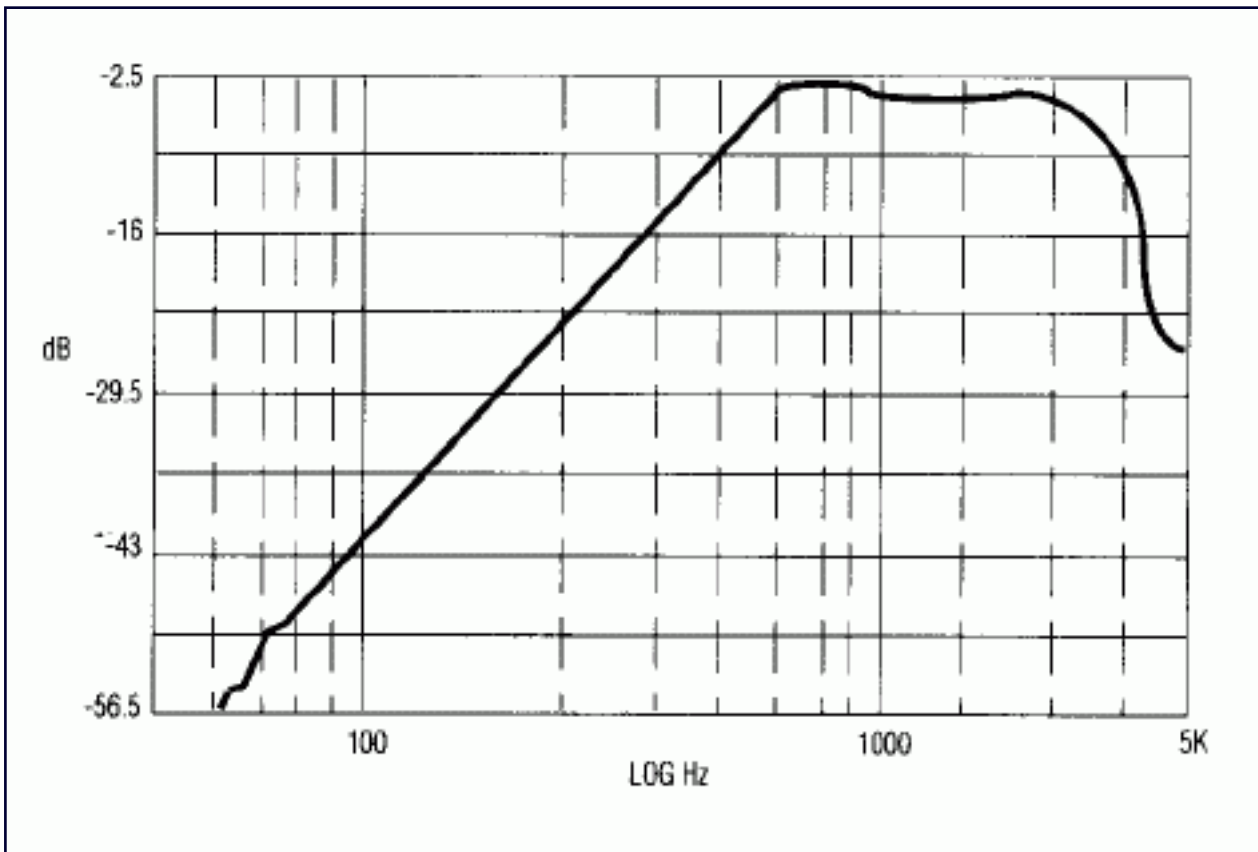


Figure 4. Circuits in Figure 1 and Figure 2 produce the same frequency response.

In both filter circuits (Figure 1 and Figure 2) the coefficients for  $f_{0A}$ ,  $f_{0B}$ ,  $Q_A$ ,  $Q_B$  were calculated by software available from Maxim (see data sheet). **Figure 4** shows the filter transfer function for either realization.

Application Note 11: <http://www.maxim-ic.com/an11>

#### More Information

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

#### Related Parts

MAX262: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN11, AN 11, APP11, Appnote11, Appnote 11

Copyright © by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>