

APPLICATION NOTE 3843

±15V Switch-Mode Power Supply Has Wide Input-Voltage Range

Abstract: This switch-mode power supply provides ±15V at 0.5A output from a 4.5V to 12V input-voltage range. The wide input-voltage range allows this power supply the flexibility to be powered from a regulated DC voltage, or even an unregulated DC voltage such as the rectified output from an inexpensive AC step-down transformer.

The power supply consists of a MAX668 boost circuit and a MAX1846 inverting circuit. Each circuit operates at a 300kHz switching frequency as a compromise among cost, size, and performance. Both circuits limit the maximum switch current, which ultimately limits the output current for a given input voltage. However, the maximum output current increases as the input voltage increases.

The MAX668 circuit in **Figure 1** contains a few components in addition to the minimum circuit implementation. C7 adds a pole to compensate for the ESR-zero of the output capacitor. R5 and C8 filter the current-sense voltage to prevent high-frequency switching noise from tripping the current limit. This is in addition to the internal 60ns current-sense blanking time.

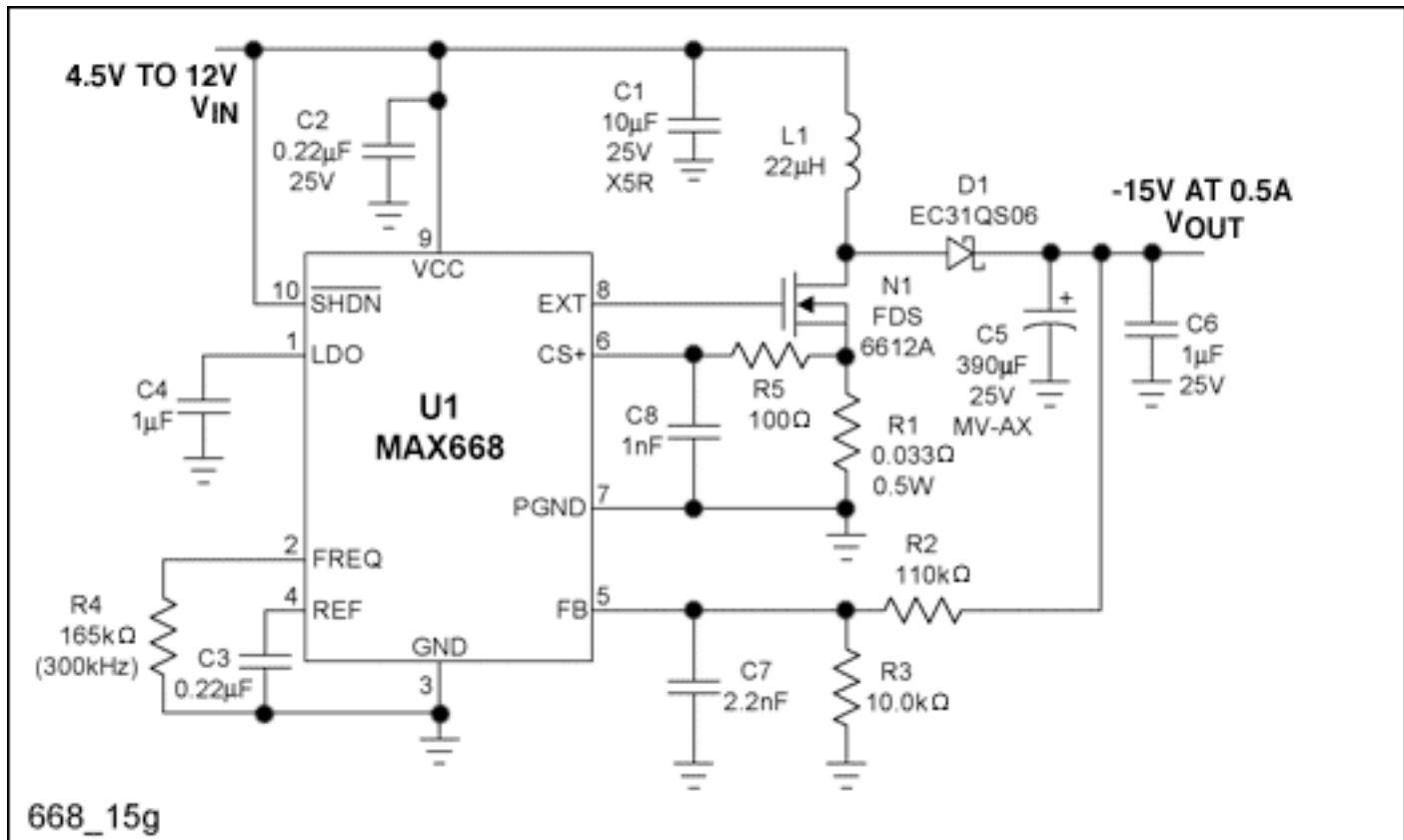


Figure 1. MAX668 Boost circuit for +15V at 0.5A.

The MAX668 output voltage can be changed to +12V by changing R2 to 86.6kΩ. The minimum input voltage then decreases to approximately 10V. No other changes are required because the MAX668 has internal compensation.

The output ripple voltage caused by switching can be reduced an order of magnitude with a secondary output filter set to one-tenth of the switching frequency. A 1Ω, 0.5W resistor placed in series with a 10μF 25V capacitor with less than 100mΩ ESR is sufficient. This introduces an additional 0.5V decrease in output voltage for a 0.5A

load. The feedback voltage must be sensed before the secondary filter for the MAX668 to work properly.

The MAX1846 circuit (**Figure 2**) also contains a few components in addition to the minimum circuit implementation. Like the C7 for the MAX668, C20 adds a pole to compensate for the ESR-zero of the output capacitor. As with the MAX668, R16 and C22 filter the current-sense voltage to prevent high-frequency switching noise from tripping the current limit. This is in addition to the internal 100ns current-sense blanking time. The MAX1846 EXT pin has a controlled slew rate that inherently limits the high-frequency switching noise.

Table 1. MAX668 Application Circuit Capabilities

| V _{IN} | I _{IN} | V _{OUT} | I _{OUT} | Efficiency |
|-----------------|-----------------|----------------------|------------------|------------|
| 5.00 | 0.0007 | 15.11 | 0 | |
| 5.00 | 1.597 | 14.81 | 0.50 | 0.927 |
| 6.00 | 1.318 | 14.85 | 0.50 | 0.939 |
| 8.00 | 0.981 | 14.91 | 0.50 | 0.950 |
| 10.00 | 0.781 | 14.96 | 0.50 | 0.958 |
| 11.00 | 0.708 | 14.98 | 0.50 | 0.962 |
| 12.00 | 0.648 | 15.01 | 0.50 | 0.965 |
| 4.47 | 1.800 | 14.78 | 0.50 | 0.918 |
| 20MHz BW | | 240mV _{p-p} | | |
| 4.46 | 2.556 | 14.70 | 0.70 | 0.903 |
| Current limit | | | ~0.71 | |

BILL OF MATERIALS

4.5V to 10V Input

15V at 0.5A Output

668_15g

| DESIGNATION | QTY | DESCRIPTION |
|-------------|----------|--|
| C1 | 1 | 10μF, 25V X5R ceramic capacitor (1210) Taiyo Yuden TMK325BJ106MM |
| C2 | 1 | 0.22μF, 25V ceramic capacitor (0805) Taiyo Yuden UMK212BJ224MG |
| C3 | 1 | 0.22μF, 10V ceramic capacitor (0603) Taiyo Yuden EMK107BJ224MA |
| C4 | 1 | 1μF, 10V X5R ceramic capacitor (0603) Taiyo Yuden LMK107BJ105MA |
| C5 | 1 | 390μF, 25V aluminum electrolytic capacitor Sanyo 25MV390AX |
| C6 | 1 | 1μF, 25V X5R ceramic capacitor (1206) |
| C7 | 1 | 2.2nF ceramic capacitor (0603) |
| C8 | 1 | 1nF ceramic capacitor (0603) |
| D1 | 1 | 3A, 60V Schottky diode Nihon EC31QS06 |
| L1 | 1 | 22μH, 6A power inductor Coilcraft DO5022P-223 |
| N1 | 1 | 30mΩ, 30V n-channel MOSFET (SO-8) Fairchild FDS6612A |
| R1 | 1 | 0.033Ω, 0.5W, 5% resistor (2012) |
| R2 | 1 | 110kΩ, 1% resistor (0603) |
| R3 | 1 | 10.0kΩ, 1% resistor (0603) |
| R4 | 1 | 165kΩ, 1% resistor (0603) |
| R5 | 1 | 100Ω, 5% resistor (0603) |
| U1 | 1 | MAX668EUB (10-μMAX®) |

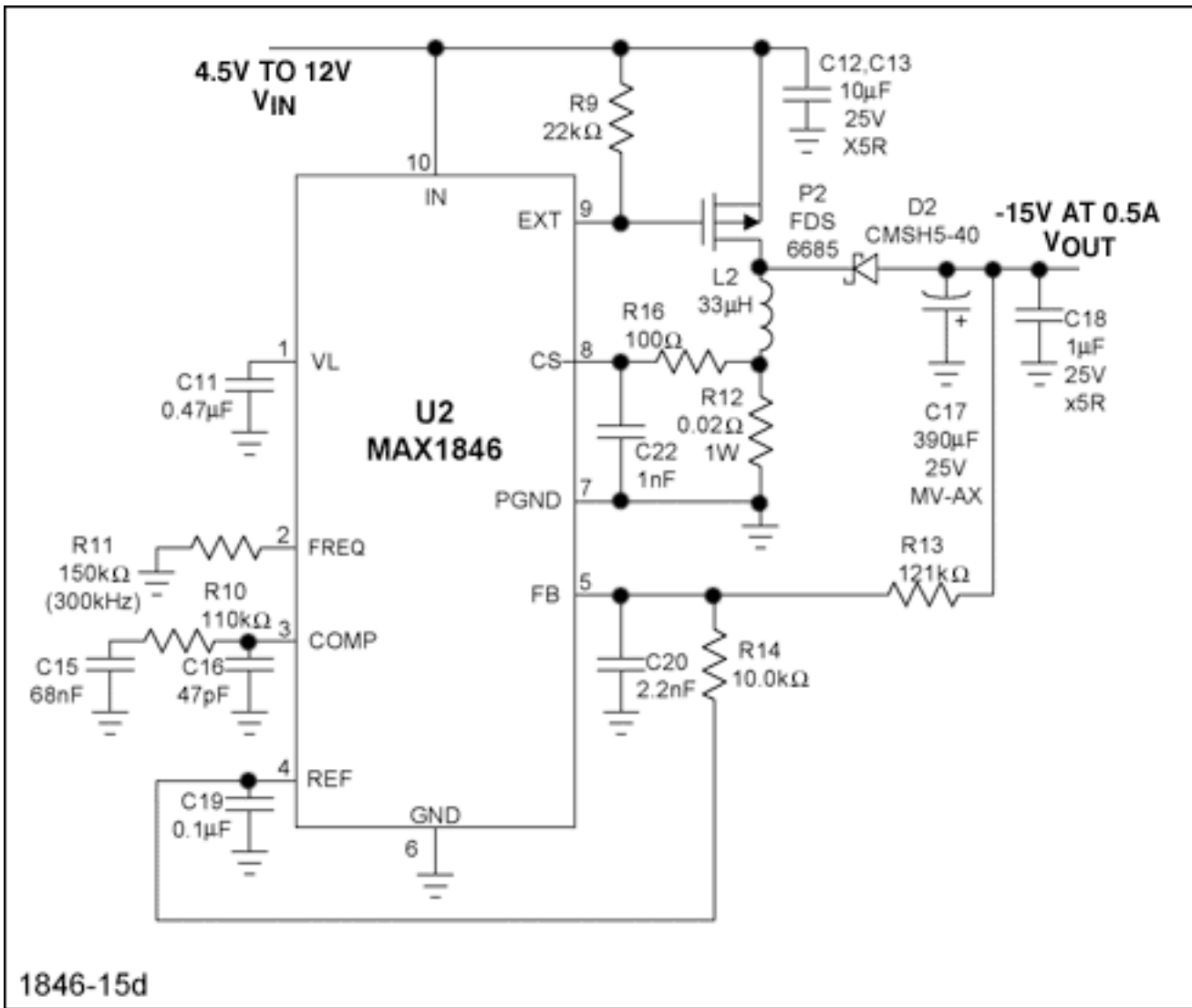


Figure 2. MAX1846 circuit for -15V at 0.5A.

The MAX1846 output voltage can be changed to -12V by changing R13 to 97.6kΩ and R10 to 91kΩ. The maximum input voltage does not decrease, though duty cycle jitter increases somewhere between 10V and 12V input. Again, the output ripple voltage caused by switching can be reduced an order of magnitude with the same secondary filter described for the MAX668. The feedback voltage must be sensed before the secondary filter for the MAX1846 to work properly.

Table 2. MAX1846 Application Circuit Capabilities

| V _{IN} | I _{IN} | V _{OUT} | I _{OUT} | Efficiency |
|-----------------|-----------------|----------------------|------------------|------------|
| 5.00 | 0.0077 | -15.15 | 0 | |
| 5.00 | 1.76 | -15.15 | 0.50 | 0.861 |
| 6.01 | 1.42 | -15.15 | 0.50 | 0.888 |
| 8.01 | 1.05 | -15.15 | 0.50 | 0.901 |
| 10.00 | 0.84 | -15.15 | 0.50 | 0.902 |
| 12.00 | 0.70 | -15.15 | 0.50 | 0.902 |
| 4.48 | 2.04 | -15.15 | 0.50 | 0.829 |
| 20MHz BW | | 360mV _{p-p} | | |
| 4.48 | 3.63 | -15.15 | 0.80 | 0.745 |
| Current limit | | | ~0.81 | |

BILL OF MATERIALS
4.5V to 12V Input
-15V at 0.5A Output
1846-15d

| DESIGNATION | QTY | DESCRIPTION |
|-------------|----------|--|
| C11 | 1 | 0.47 μ F ceramic capacitor (0603) |
| C12,C13 | 2 | 10 μ F, 25V X5R ceramic capacitor (1210) Taiyo Yuden TMK325BJ106MM |
| C15 | 1 | 68nF ceramic capacitor (0603) |
| C16 | 1 | 100pF ceramic capacitor (0603) |
| C17 | 1 | 390 μ F, 25V aluminum electrolytic capacitor Sanyo 25MV390AX |
| C18 | 1 | 1 μ F, 25V X5R ceramic capacitor (1206) |
| C19 | 1 | 0.1 μ F ceramic capacitor (0603) |
| C20 | 1 | 2.2nF ceramic capacitor (0603) |
| C22 | 1 | 1nF ceramic capacitor (0603) |
| D2 | 1 | 5A, 40V Schottky diode Central Semi CMSH5-40 |
| L2 | 1 | 33 μ H, 5A inductor Coilcraft DS5022P-333 |
| P2 | 1 | 35m Ω , -30V p-channel MOSFET (SO-8) Fairchild FDS6685 |
| R9 | 1 | 22k Ω , 5% resistor (0603) |
| R10 | 1 | 110k Ω , 5% resistor (0603) |
| R11 | 1 | 150k Ω , 5% resistor (0603) |
| R12 | 1 | 0.02 Ω , 1W, 1% resistor (2512) Dale WSL-2512-R020-F |
| R13 | 1 | 121k Ω , 1% resistor (0603) |
| R14 | 1 | 10.0k Ω , 1% resistor (0603) |
| R16 | 1 | 100 Ω , 5% resistor (0603) |
| U2 | 1 | MAX1846EUB (10-μMAX) |

Application Note 3843: www.maxim-ic.com/an3843

More Information

For technical support: www.maxim-ic.com/support

For samples: www.maxim-ic.com/samples

Other questions and comments: www.maxim-ic.com/contact

Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest?
[Sign up for EE-Mail™.](#)

Related Parts

MAX1846: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX668: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN3843, AN 3843, APP3843, Appnote3843, Appnote 3843

Copyright © by Maxim Integrated Products

Additional legal notices: www.maxim-ic.com/legal

