

## SHORT CIRCUIT PROTECTION ON L6203

by G. Scrocchi and G. Fusaroli

With devices like L6203 used as driver often interfacing the external world by means of wires, can be easy to have short circuits.


A short circuit can occur for many reasons : a short on the load, a mistake during the connection of the wires between the device and the load (i.e. L6203 driving a motor), an accidental short between the wires and so on. The outputs of L6203 are not protected against the short circuit and if a short occurs, the big amount of current flowing through the outputs can destroy the device.

To avoid this risk can be useful to add a circuitry to protect the device : in this case, to have a total protection, we must consider three types of short circuit :


- 1 - output to output short circuit
- 2 - output to supply voltage short circuit
- 3 - output to ground short circuit

The first step is to sense the short circuit current. In output to output (fig 1) or output to supply (fig 2) short circuit can be used the sensing resistor ( $R_{SL}$ ) already used to set the current flowing in the load during the normal operation.

**Figure 1.**

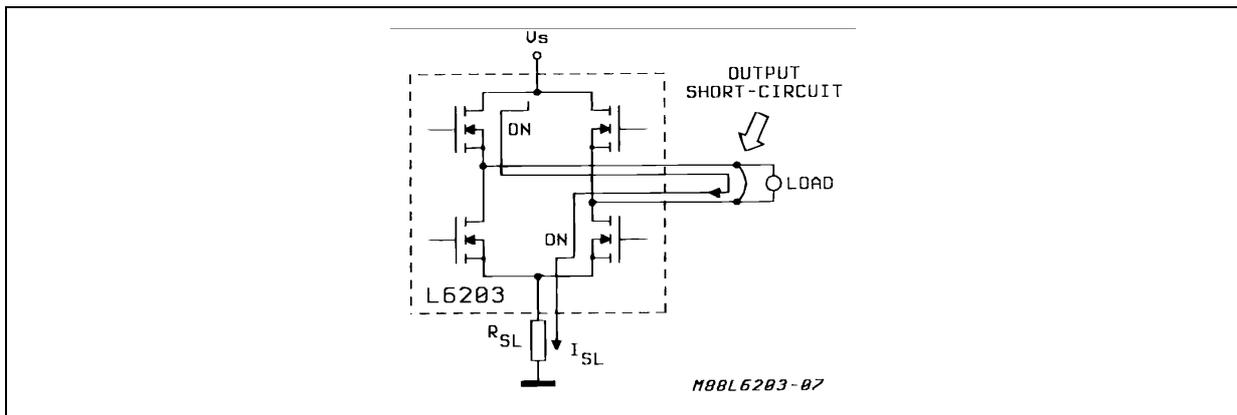

**Figure 2.**

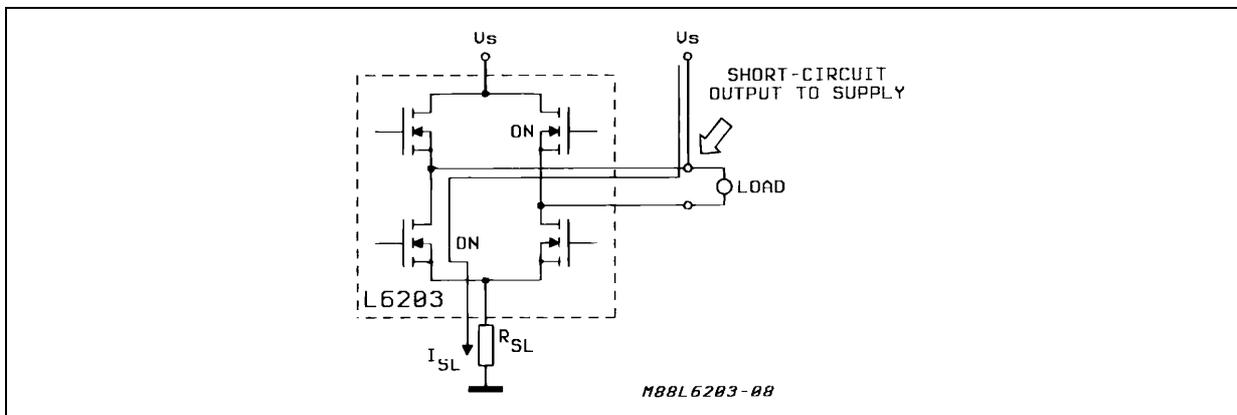



$$I_{SL} > \frac{V_D + V_{THSCMT}}{R_{SC}} = \frac{0.6 + 0.7}{0.165} = 7.8A$$

The effective short circuit peak current is greater than  $I_{SU}$  and  $I_{SL}$  : this is due to the high  $di/dt$  during the short and to the delay between the short circuit detection and the ENABLE intervention :


$R_{SU}$  and  $R_{SL}$  must be non inductive resistors.

$R_1$  and  $R_2$  are used to scale the signal when the transistor goes on and in conjunction with  $C_1$  to filter the short circuit signals in order to avoid false trigger of the SCR : this filtering should not be too much heavy to avoid to introduce an excessive delay in the short circuit loop.

$I_{SU}$  and  $I_{SL}$  must be calculated at the effective operating temperature being the  $V_{be}$  and  $V_d$  temperature dependent.

Instead of the SCR, a monostable with a long time constant (0.3 , 0.5 sec) can be used : in the case, every time a short circuit occurs, L6203 is disabled for the monostable time constant and then enabled, if the short is still present L6203 is disabled again, if the short was removed L6203 returns in normal operation (fig 5).

Figure 5.

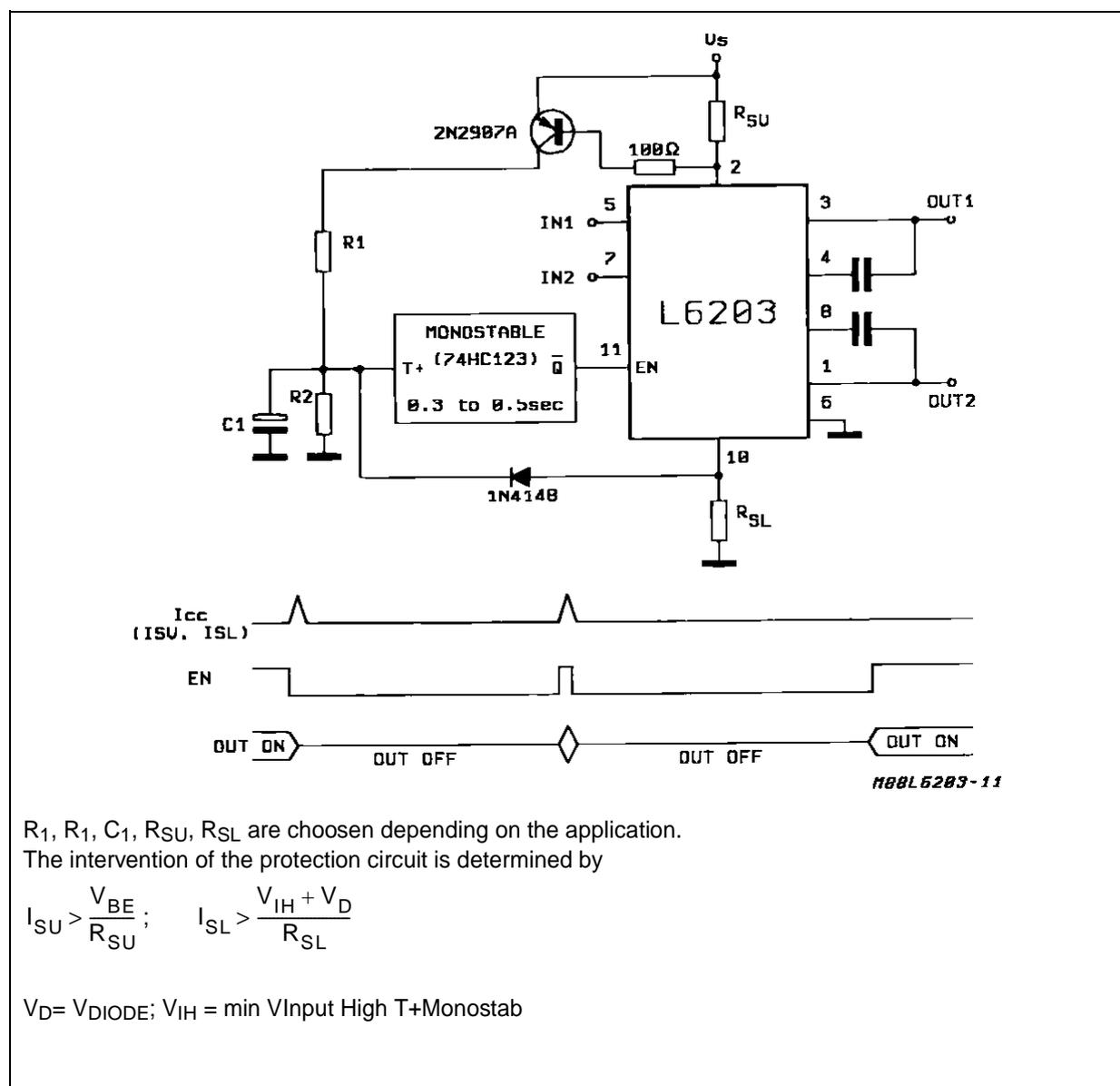

$R_1, R_2, C_1, R_{SU}, R_{SL}$  are chosen depending on the application.

The intervention of the protection circuit is determined by

$$I_{SU} > \frac{V_{BE}}{R_{SU}} ; \quad I_{SL} > \frac{V_{IH} + V_D}{R_{SL}}$$

$V_D = V_{DIODE}; V_{IH} = \min V_{Input High T+Monostab}$

Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

The ST logo is a registered trademark of STMicroelectronics.  
All other names are the property of their respective owners

© 2003 STMicroelectronics - All rights reserved

**STMicroelectronics GROUP OF COMPANIES**

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan -  
Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States  
[www.st.com](http://www.st.com)