



AN2097 APPLICATION NOTE

VIpower: 10W POWER SMPS USING VIPer22A FOR AIR-CONDITIONER APPLICATION

1. ABSTRACT

New air-conditioner systems use two main low-voltage outputs to supply the internal electronic equipment, respectively these values are +12V and +5V. These low output voltages are generated by a switch mode power supply. Many important features are requested by the power supply: high efficiency, light weight with compact size and low power consumption in stand-by condition just to mention some of them.

VIperX2 family allows to develop power supply having all these features together hence these devices are a suitable solution to develop air-conditioner applications. Specifically, the board shown here following has been developed in order to improve the features explained in figure 1.

The application, mentioned in this note, complains the technical specifics summarized in table 1.

Figure 1. Board Layout

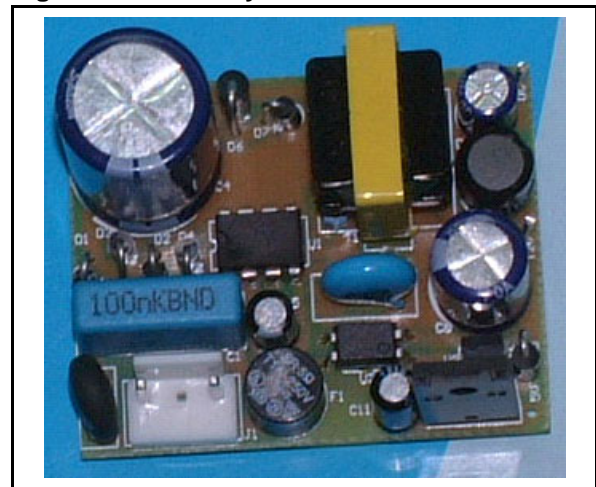


Table 1. Electrical Specification

| | |
|---------------------------|---|
| Input AC range | 85-265 V _{ac} |
| Output 1 | 12V |
| Output 2 | 5V/400mA (linear regulator from output 1) |
| Ripple | <50mV |
| Output current (12V & 5V) | 800mA - continuous |
| | 900mA - peak, less than 5 minutes |
| Stand-by consumption | <1W |

1. VIPERX2A DESCRIPTION

The VIPerX2A family combines a dedicated current mode PWM controller with a high voltage Power MOSFET, on the same monolithic chip, within one package only. That allows to obtain a components reduction achieving a cost reduction and a design and PCB simplification. For these reasons this family is widely used in many off-line switching mode power supplies. Furthermore, a tiny size package for SMD technology is available (SO-8). VIPer family is able to meet the Blue Angels and Energy Star standards in matter of stand-by power consumption (less than 1W).

1.1. General Features

The VIPerX2A devices are built in the proprietary VIpower M0-3 H.V.

The M0-3 H.V. technology allows to put the low voltage systems (PWM) and the power stage with vertical current flow in the same chip by means of a P-type buried layer, as illustrated in figure 2.

The VIPerX2A devices have the below general features:

- Automatic thermal shutdown.
- High voltage start-up current source.
- HICCUP mode in order to avoid the break-down condition for output short circuits.
- Burst mode to assure low-power consumption in low-load condition.

AN2097 - APPLICATION NOTE

Moreover, VIPower M0-3 Technology allows to develop Power MOSFETs able to guarantee a minimum breakdown voltage of 730V. Table 2

shows the device power capability, in different packages and different work conditions.

Figure 2. M0-3 Technology


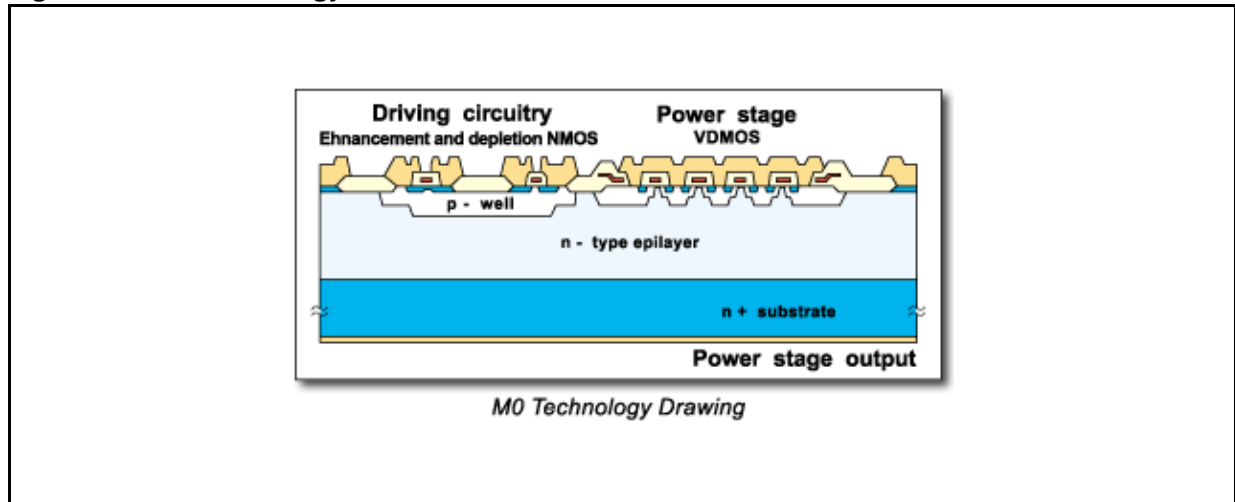


Table 2. Power Capability for Different Input Range and Different Package

| | Wide Range (85-265V) | | Single Range (180-265V) | |
|----------|----------------------|-----|-------------------------|-----|
| | SO-8 | DIP | SO-8 | DIP |
| VIPer12A | 5W | 8W | 8W | 13W |
| VIPer22A | 7W | 12W | 12W | 20W |

Figure 3. Block Diagram

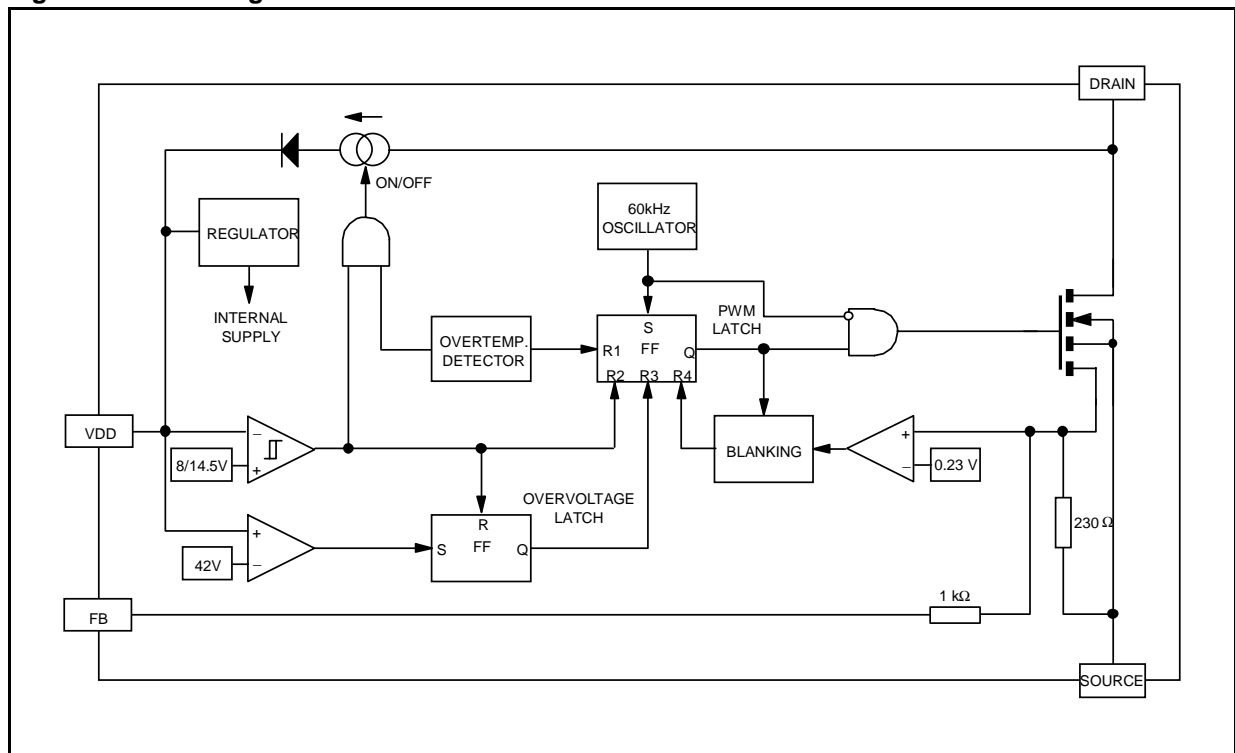

1.2. Block Diagram

Examining the block diagram in figure 3, it is possible to observe that the power section is driven by a current mode structure with a fast comparator using the current delivered by the N-MOS sense and by the feed-back pin (FB). The comparator output is connected to the Blanking Time Block in order to assure the minimum turn on time. An internal oscillator fixes the switching frequency at 60kHz, so further external component will not be necessary. Other internal blocks are the Regulator, used by internal supply and able to even support 45V on V_{DD} pin and the Over-temperature Detector to provide the thermal shutdown at 170°C typical.

The device system control is a current mode structure in which the N-MOS sense current and the FB current are summed in the resistor R2. The voltage across R2 depends on this current value and this voltage value is compared with an internal fixed voltage reference (0.23V). The comparator output drives the MOSFET, therefore the switching frequency depends on the feedback current value and the I_d value. In this application the feedback loop is implemented by driving this FB pin with the output voltage using an optocoupler in order to assure the electrical isolation between the input and the output. V_{DD} voltage is monitored by a hysteresis comparator able to manage the start-up current generator. In fact, it is switched on in order to charge the V_{DD} capacitor in as long as the V_{DD} voltage value becomes greater than the V_{DDON} value. Once this


condition is reached, the Power MOSFET starts to switch. Burst mode condition works skipping some switching cycles decreasing the power consumptions when the load becomes light.

2. AIR-CONDITIONER APPLICATION

2.1 Schematic

Figure 4 gives the schematic of the power supply with VIPer22 used in the air-conditioner application described in this note. It is designed to have two voltage outputs, respectively 12V and 5V. The maximum power capability is 10W and it is delivered on the 12V output. Peak current value of this output is 900mA. Instead, the second output (5V) is obtained connecting in the first output in cascade of a linear voltage regulator (7805) and a zener diode D9 that is used in order to share the voltage drop. This solution allows to have a very high accuracy in 5V output voltage value, therefore this solution is suitable for supplying microcontroller or/and logical circuit, LCD and buzzer. The current capability of this second output is 400mA. The solution proposed, shown in figure 4, is an isolated fly-back topology in secondary feedback. The control loop is obtained through an optocoupler, with a high stability voltage reference (TL431), in order to check the 12V output assuring the complete insulation between the input and the output. A transient snubber circuit (D6-D7), allows to have a reliable protection for spikes voltage due to the reflected voltage and the leakage inductance.

Figure 4. Air-Conditioner SMPS Schematic

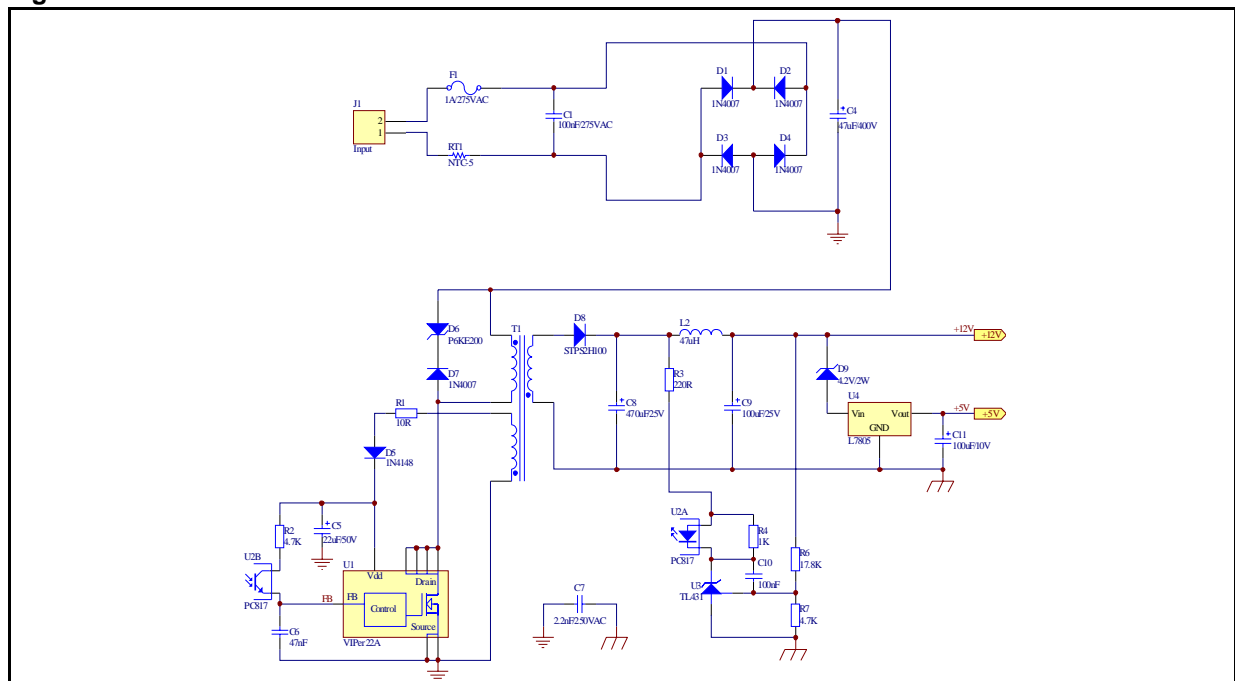

2.2 Result

The main purpose of this application is to have both the output voltages very accurate. The first one (12V) has a high accurateness because it is in secondary regulation feedback, while the second one (5V) has a high precision because this line is obtained using a standard linear regulator. This air-conditioner application is developed to work in

wide range (85-265 VAC). The stand-by power consumption is always lower than 1W, as shown in figure 5, satisfying the Energy Star rules regarding stand-by power consumption.

Instead, figure 6 shows the efficiency measurement achieved keeping the 5V output in no-load condition.

Figure 5. Power consumption in stand-by condition


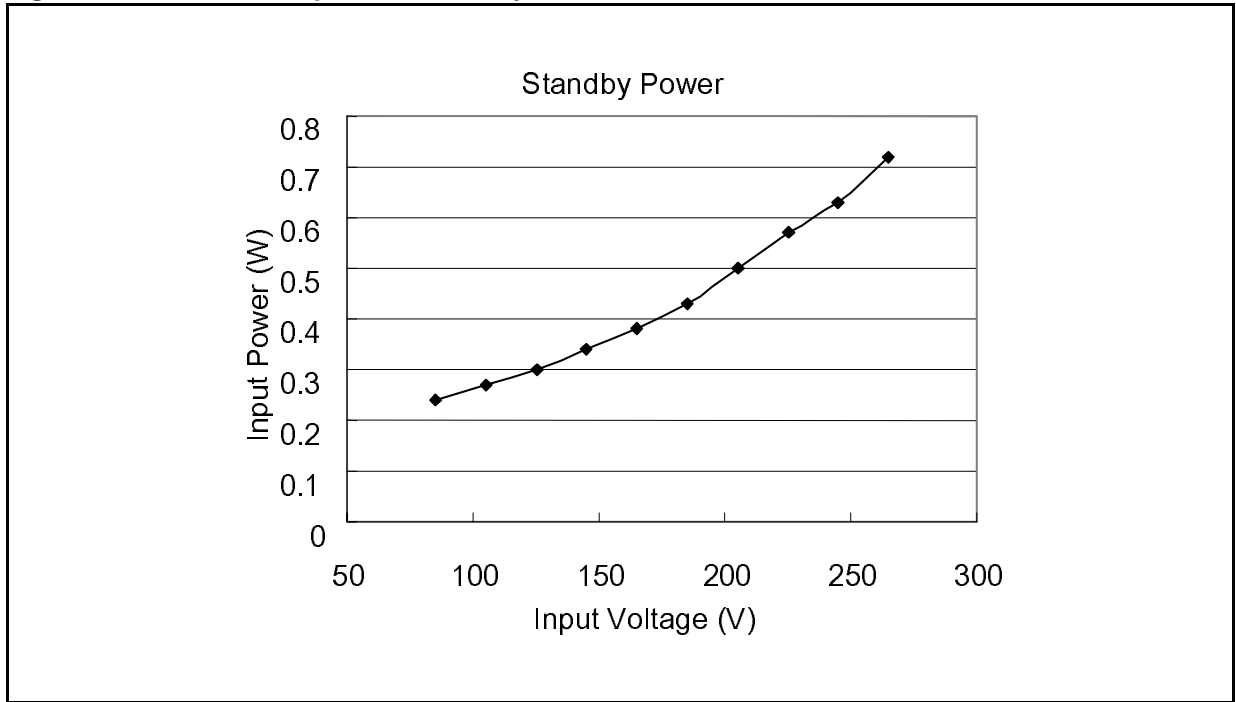


Figure 6. Efficiency measurement

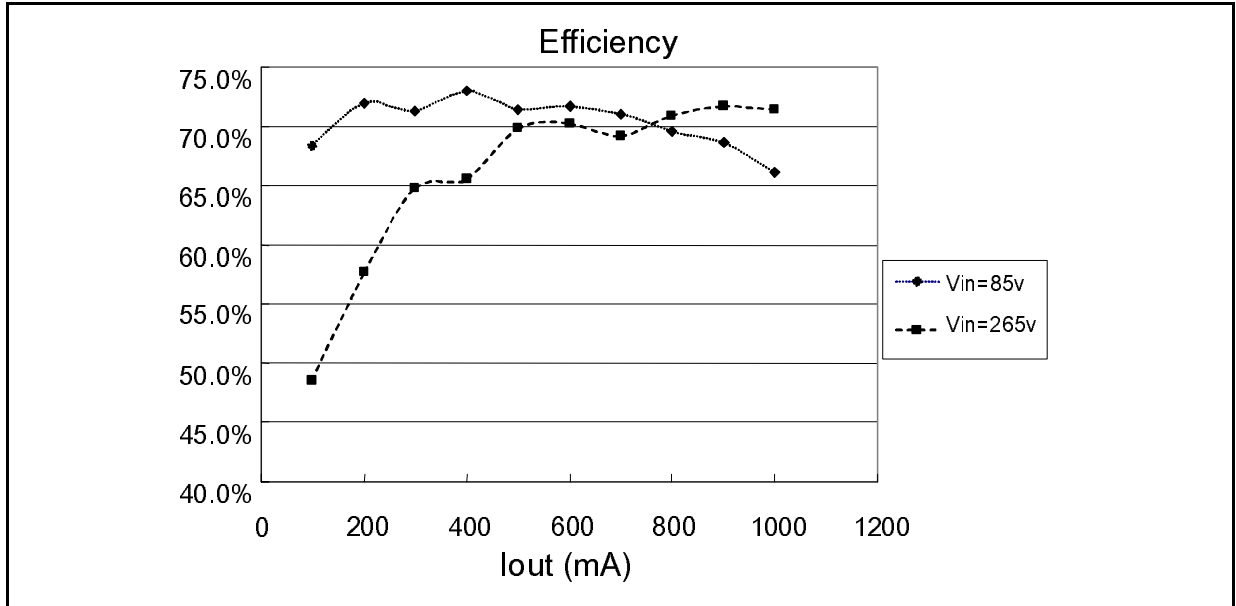


3. DEMOBOARD DESCRIPTION

3.1 Board Layout

It is a single layer type with copper on bottom side, and serigraphy on top side. Both of them are

represented in figure 7. This PCB Layout dimension is 50mm x 40mm.

Figure 7. PCB Layout (dimension is 50mmX40mm)

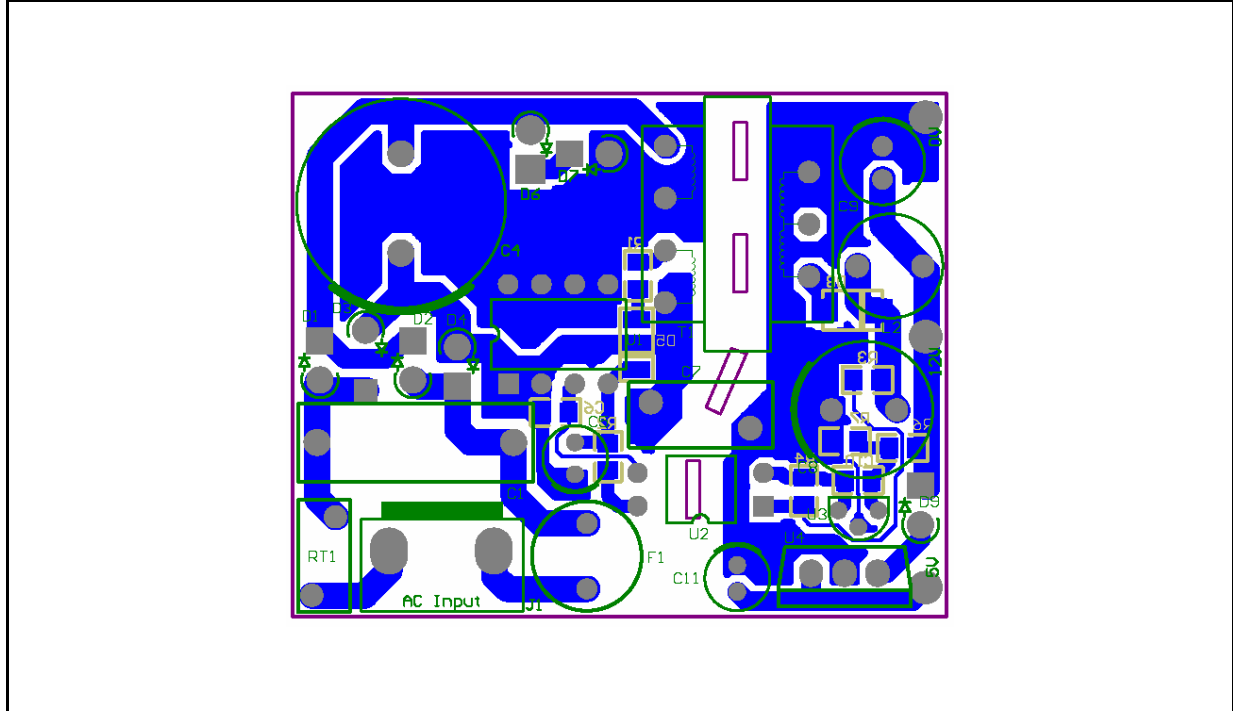

3.2 Bill of material

Table 3 gives the list of the components used to develop this application.

Table 3. Bill of Material

| Reference | Value | Description |
|-----------|------------------|--|
| C1 | 100nF/275VAC | X-Capacitor Evox Rifa |
| C4 | 47 μ F/400V | Polarized Capacitor (Radial) |
| C5 | 22 μ F/50V | Polarized Capacitor (Radial) |
| C6 | 47nF | Capacitor |
| C7 | 2.2nF/250VAC | Y-Capacitor Evox Rifa |
| C8 | 470 μ F/25V | Polarized Capacitor (Radial) |
| C9 | 100 μ F/25V | Polarized Capacitor (Radial) |
| C10 | 100nF | Capacitor |
| C11 | 100 μ F/10V | Polarized Capacitor (Radial) |
| D1 | 1N4007 | 1.0A General Purpose Rectifier |
| D2 | 1N4007 | 1.0A General Purpose Rectifier |
| D3 | 1N4007 | 1.0A General Purpose Rectifier |
| D4 | 1N4007 | 1.0A General Purpose Rectifier |
| D5 | 1N4148 | 80V-0.5A Schottky Diode |
| D6 | P6KE200 | STMicroelectronics Zener Diode |
| D7 | 1N4007 | Default Diode |
| D8 | STPS2H100 | STMicroelectronics 100V-2A Power Schottky Diode |
| D9 | 4.2V/2W | Zener Diode |
| F1 | 1A/275VAC | Fuse |
| J1 | Input | Header, 2-Pin |
| L2 | 47 μ H | Inductor |
| R1 | 10R | Resistor |
| R2 | 4.7K Ω | Resistor |
| R3 | 220R | Resistor |
| R4 | 1K | Resistor |
| R6 | 17.8K Ω | Resistor |
| R7 | 4.7K Ω | Resistor |
| RT1 | NTC-5 | NTC Resistor |
| T1 | | Three-winding Transformer (Non-Ideal) |
| U1 | VIPer22A | STMicroelectronics Off Line SMPS |
| U2 | PC817 | Photocoupler Sharp |
| U3 | TL431 | STMicroelectronics Programmable Voltage Reference |
| U4 | L7805 | STMicroelectronics 1A Voltage Regulator |

3.3 Transformer Parameters


The transformer used in this SMPS for air-conditioner application is wound in E19 core. The

electrical, mechanical and winding specifications are given in table 4 and figure 8.

Table 4. Transformer parameters

| Core size: E19/8/5 | | |
|--------------------|--------------------|--------|
| Primary Winding | Primary Inductance | 3.0mH |
| | Turns | 133 |
| | Coil | 0.25mm |
| Auxiliary Winding | Turns | 21 |
| | Coil | 0.25mm |
| Secondary Winding | Turns | 17 |
| | Coil | 0.6mm |

Figure 8. Transformer Structure Description

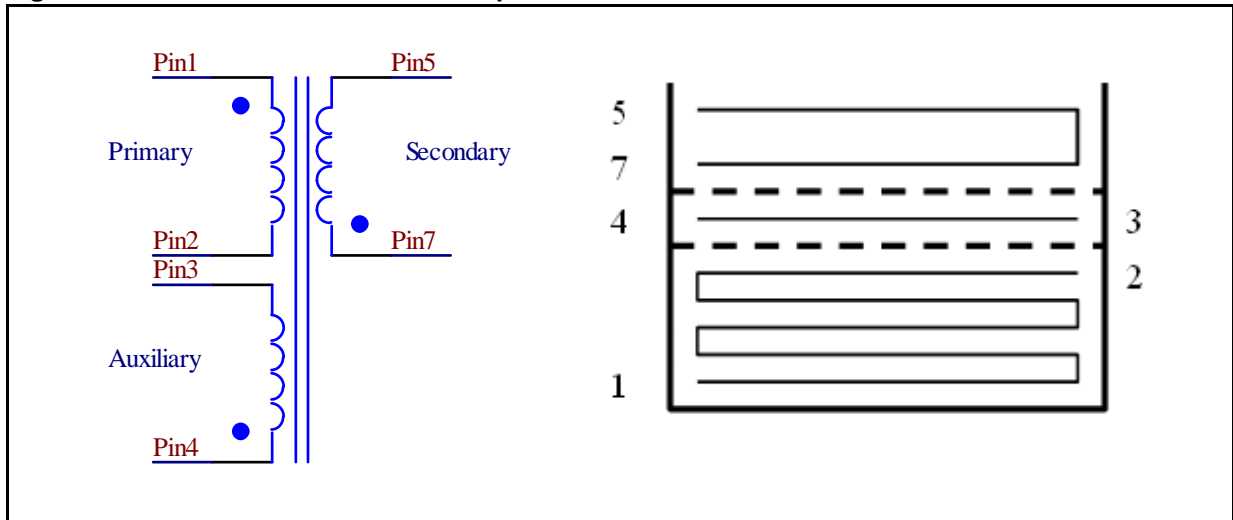

Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

The ST logo is a registered trademark of STMicroelectronics.
All other names are the property of their respective owners

© 2004 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan -
Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com