
LP3985 MicroSMD-5 **Evaluation Board** Instruction

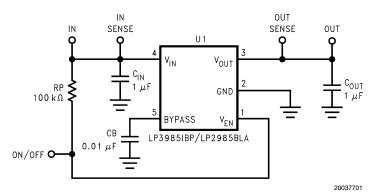
National Semiconductor Application Note 1219 Mary F Kao May 2002



This evaluation board is designed to enable independent evaluation of the LP3985 electrical performances. Each board is assembled and tested in the factory. This evaluation board instruction is for the microSMD-5 large bump and small bump packages.

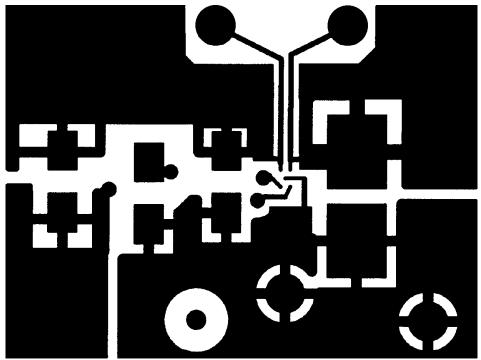The schematic and layout of the evaluation board are given





20037702

Note: The board layout for the large bump and the small bump microSMD-5 is the same. Only the footprints are different.

The LP3985 is a micropower CMOS voltage regulator that can provide up to 150 mA of output current. The 0.01 μF bypass capacitor is optional; but if used, it will reduce noise on the regulator output. The RP resistor is tied to $\ensuremath{V_{\text{IN}}}$ so that the regulator is on all the time. To control the V_{EN} pin externally, disconnect RP resistor and use the ON/OFF connector on the evaluation board.

The input sense and output sense pins are used for more precise voltage measurements. These pins are connected to the LP3985 input and output via high impedance traces.

The LP3895 is also available in SOT23-5. An evaluation board for the SOT23-5 package is available as well.

Below is the bill of material for the LP3985 microSMD-5

Designator	Value	Amount	Footprint	Note
RP	100 kΩ	1	0805	
СВ	0.01 μF	1	0805	
C _{IN}	1 μF	1	0805	X5R or X7R
C _{OUT}	1 μF	1	0805/1812	X5R or X7R
U1	LP3985IBP-xx, or	1	BPA05CMC or	The "xx" corresponds to the appropriate LDO output
	LP3985IBL-xx		BLA05ADC	voltage option.
Test Pins		7		Keystone 1040

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- 1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



www.national.com

National Semiconductor Europe

Fax: +49 (0) 180-530 85 86 Email: europe.support@nsc.com Deutsch Tel: +49 (0) 69 9508 6208 English Tel: +44 (0) 870 24 0 2171

Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Response Group Tel: 65-2544466

Fax: 65-2504466 Email: ap.support@nsc.com **National Semiconductor** Tel: 81-3-5639-7560 Fax: 81-3-5639-7507