

# DN88

## The ZXCT1030 current monitor used as a GPS antenna switch with short circuit protection

Duane Gibbs, Field Applications Engineer

---

### Introduction

High side current monitors such as the Zetex [ZXCT1030](#) were developed to enable the measurement of current on the supply side of a circuit versus the ground return path. They are often used in the output of a power supply or motor drive to determine if excess current is flowing and to take evasive action such as shutting down the supply or motor drive circuit. Another type of application for the current monitor is described in this design note where the current in a signal path is used to detect an active GPS antenna and automatically switch the RF path

### Application

Most GPS navigation systems are equipped with an internal GPS antenna but sometimes it is desirable to use an external active antenna for improved performance or to place the antenna at a distance from the equipment such as on the roof of a car. In this case the user of the system would plug an active GPS antenna into an external jack on the navigation system and place the antenna in the desired location. In the past the user then had to cause the circuit to switch over to the external antenna via a switch or software selection. In addition short circuit protection is needed on the external antenna jack in case the user applies a short or a faulty antenna. This has historically been accomplished using discrete components to detect an over current condition on the active antenna power line.

### Description

This design note shows a method of accomplishing both RF path switching and short circuit protection with the ZXCT1030 current monitor. Refer to Figure 1 for this description of circuit details and operation. U1 is the current monitor, U2 is a typical RF switch and U3 is an optional comparator added for an OCP (over-current protection) error flag. A sense resistor R5 is inserted in the active antenna power supply path and the current monitor U1 senses the voltage across R5. The ZXCT1030 has an open collector comparator and voltage reference integrated in the package. In this application the comparator output is used to switch the RF path between antennas.

### Antenna switching

The comparator output 'VCOUT' is brought out on pin 8 and its inverting input 'VCOMP' is available on pin 5. The ZXCT1030 has an internal 1.24V reference 'VREF' that is brought out on pin 6. A voltage divider is formed by R3 and R4 to provide a 100mV reference level at 'VCOMP', which represents 10mA of current flow to the external antenna. The 10mA level was chosen to be below the range of current draw of active antennas, typically 20mA to 35mA. The comparator has an open collector active low output that is asserted when  $V_{sense} \times Gain > V_{comp}$ , where  $Gain = 10$ . When the current passes 10mA,  $V_{sense} \times 10 > 100mV$  and the output on pin 8 is asserted low. The comparator output is pulled up to the 3.3V rail via R1 and R8 and the output switches from 3.3V to 0V when asserted. This output is connected to the CNTL input of the UPG2012 RF switch at U2 and causes the connection to be made between the external antenna and the

# DN88

receiver as shown. When no external antenna is connected, the CNTL input is high and the connection is made between the internal antenna and the receiver.

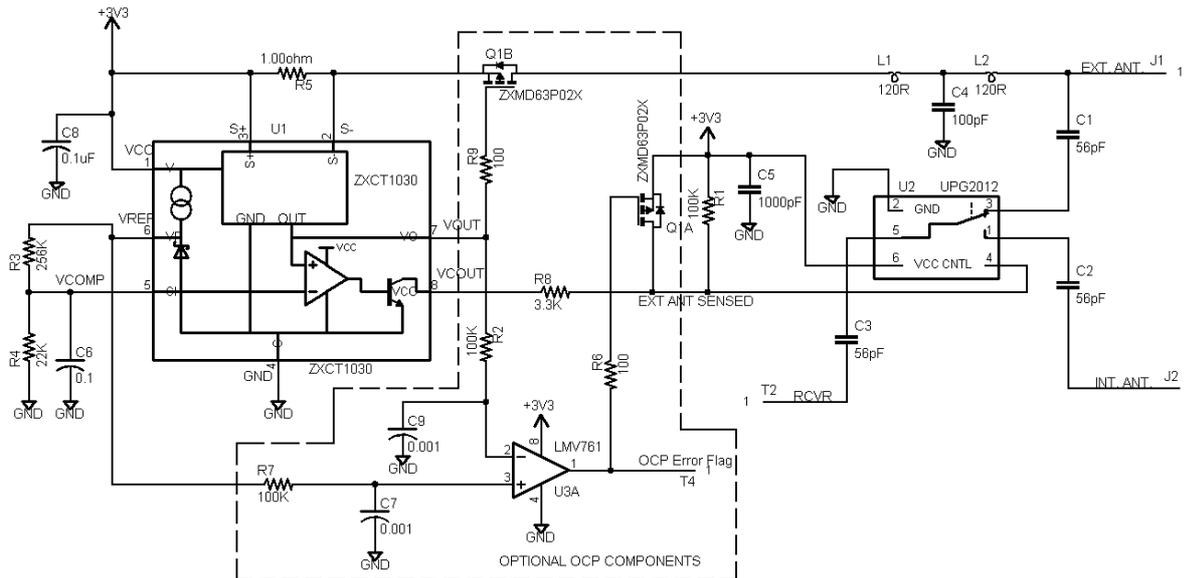


Figure 1 - ZXCT1030 RF path switching with optional over-current protection

## Optional over-current protection

An analog voltage 'VOUT' that is proportional to the current flow through sense resistor R5 is available from the ZXCT1030 on pin 7. This output is used for short circuit protection in this design. Another comparator U3 has been added to create an error flag for a processor and to automatically switch back to the internal antenna when there is a short on the external jack. VOUT is applied to U3's inverting input via R2 and the 1.24V reference level from VREF is applied to its non-inverting input via R7. When the current through Rsense exceeds 124mA, VOUT will exceed 1.24V and the U3 output will assert low. In addition to acting as an error flag, this output is connected to the gate of Q1A via R6. Q1 is a dual P channel MOSFET package ZXMD63P02X. Q1A will apply a low resistance across the R1 pull up resistor causing U2's CNTL input to return high and the internal antenna to be reconnected. U3, Q1A and associated passive components are optional and only needed if it is desired to have uninterrupted operation when a shorted antenna is applied to the external antenna jack.

The second P channel MOSFET Q1B is located in the 3.3V rail and its gate is connected to VOUT via resistor R9. As the current increases due to an over current condition in the external antenna connection, VOUT reduces the gate to source voltage causing the Q1B channel resistance to increase. Short circuit current is limited below 200mA from the 3.3V source into a shorted external antenna by this method.

## Conclusion

The flexibility of the ZXCT1030 current monitor was demonstrated in this application. It was used to perform two functions in this example. This design note showed how a current monitor can be used to detect a circuit configuration change, in this case an external antenna being plugged into a GPS navigation system, and make an automatic circuit change. In addition the second function of over current protection was added with minimal additional parts reducing the discrete component count.

# DN88

---

## Definitions

### Product change

Zetex Semiconductors reserves the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

### Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Zetex with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Zetex does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

### Life support

Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Zetex Semiconductors plc. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

---

### Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

---

### Terms and Conditions

All products are sold subjects to Zetex' terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Zetex sales office .

---

### Quality of product

Zetex is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Zetex Semiconductors or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: [www.zetex.com/salesnetwork](http://www.zetex.com/salesnetwork)

Zetex Semiconductors does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

---

### ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

---

### Green compliance

Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

---

### Product status key:

"Preview"	Future device intended for production at some point. Samples may be available
"Active"	Product status recommended for new designs
"Last time buy (LTB)"	Device will be discontinued and last time buy period and delivery is in effect
"Not recommended for new designs"	Device is still in production to support existing designs and production
"Obsolete"	Production has been discontinued

---

### Datasheet status key:

"Draft version"	This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.
"Provisional version"	This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice.
"Issue"	This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.

---

### Zetex sales offices

Europe	Americas	Asia Pacific	Corporate Headquarters
Zetex GmbH Kustermann-park Balanstraße 59 D-81541 München Germany Telephone: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com	Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788 USA Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com	Zetex (Asia Ltd) 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com	Zetex Semiconductors plc Zetex Technology Park, Chadderton Oldham, OL9 9LL United Kingdom Telephone: (44) 161 622 4444 Fax: (44) 161 622 4446 hq@zetex.com

---

© 2007 Published by Zetex Semiconductors plc